

Physics

Semester 2

Weeks 5 - 6

Monday (February 2nd)

- See last week Thursday

Tuesday (February 3rd)

- Shutdown Day

Wednesday / Thursday (February 4 – 5)

- Worksheet day

Journal 4.3

- What are my post secondary educational plans?

- **T:** [6A](#) - Use scientific notation and predict how the magnitude of the electric force between two objects depends on their charges and the distance between their centers using Coulomb's law.
- [6C](#) - Investigate and describe conservation of charge during the process of induction, conduction, and polarization using different materials such as electroscopes, balloons, rods, fur, silk and Van der Graaf generators.
- **O:** I will continue to learn about static charge
- **D:** by beginning a group project that will be a major grade presentation.
- **A:** Coulomb's law
- **Y:** What methods of research and writing will ensure that I earn a good grade on my project?

Friday (February 6th)

- C-Day

Monday / Tuesday (February 9 – 10)

- Continue projects
- Practice presentation

- **T:** [6A](#) - Use scientific notation and predict how the magnitude of the electric force between two objects depends on their charges and the distance between their centers using Coulomb's law.
- [6C](#) - Investigate and describe conservation of charge during the process of induction, conduction, and polarization using different materials such as electroscopes, balloons, rods, fur, silk and Van der Graaf generators.
- **O:** I will continue to learn about static charge
- **D:** by working on my electrostatics project
- **A:** Coulomb's law
- **Y:** What are the requirements for a good grade on the project?

Wednesday / Thursday (February 11 – 12)

- Presenting projects

- **T:** [6A](#) - Use scientific notation and predict how the magnitude of the electric force between two objects depends on their charges and the distance between their centers using Coulomb's law.
- [6C](#) - Investigate and describe conservation of charge during the process of induction, conduction, and polarization using different materials such as electroscopes, balloons, rods, fur, silk and Van der Graaf generators.
- **O:** I will share what I have learned with my classmates
- **D:** by presenting my project.
- **A:** Coulomb's law
- **Y:** How does my effort affect not only my grade but the grade of my classmates?

Friday (February 13th)

- No School.

Tuesday / Wednesday (Feb 17 – 18)

- Begin electrical circuits

- T: 6D - Analyze, design, and construct series and parallel circuits using schematics and materials such as switches, wires, resistors, lightbulbs, batteries, voltmeters, and ammeters.
- 6E - Calculate current through potential difference across, resistance of, and power used by electrical circuit elements connected in both series and parallel circuits using Ohm's law.
- O: I will be able to learn about electrical circuits
- D: by discussing a Page Keeley, taking notes, and solving problems.
- A: current, resistance, amperes, voltage (taking notes and discussing)
- Y: What relationship does Ohm's law provide us?

Circuits




Electric Current

- Electric Current-
 - A flow of charged particles is a current
- Conventional Current-
 - A flow from higher potential difference to lower potential difference (+ to -)
- Battery
 - Converts chemical energy to electrical
- Photovoltaic (Solar) Cell
 - Converts light to electrical



Electric Circuits

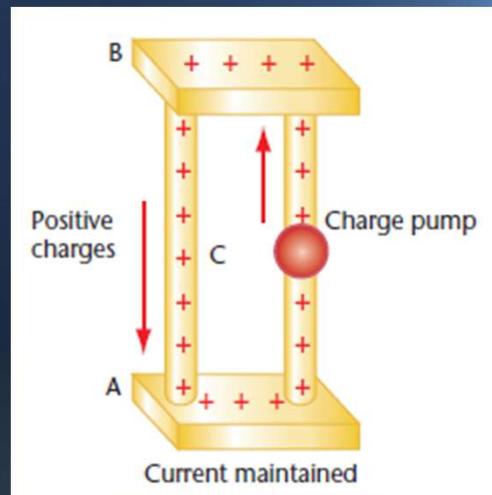- Electric Circuit
 - Closed loop that charges travel through
 - Includes charge pump which increases potential energy



Current

- Electric Current (I)
 - Rate of flow of electric charges
 - Measured in Amperes (A)
 - $I = q/t$
 - $1 \text{ A} = 1 \text{ C/s}$
 - Ammeter measures electric current



Voltage

- Voltage- Potential Difference- EMF (V)
 - Potential energy of the electrons- causes charges to move through the circuit.
 - Measured in Volts (V)
 - Voltmeter measures Voltage



Resistance

- Resistance (R)
 - Restricts the flow of current
 - Measured in Ohms (Ω) or Volts per Amp (V/A)



Resistors

- Resistors
 - produce potential differences by resisting flow of currents
 - Ex: Light bulbs, resistors
- Superconductor
 - Frozen conductors
 - Zero resistance
- Potentiometer
 - A variable resistor
 - Ex: Dimmer Switch




Power

- Power
 - Energy delivered through the circuit per second
 - P (Power) = I (Current) \times V (Voltage)
 - Measured in Watts
- Problem
 - A 6.0 V battery delivers a 0.5 A current to an electric motor. What is the power?
 - $P = (0.5 \text{ A})(6.0 \text{ V})$
 - $P = 3.0 \text{ W}$





Diagramming Circuits

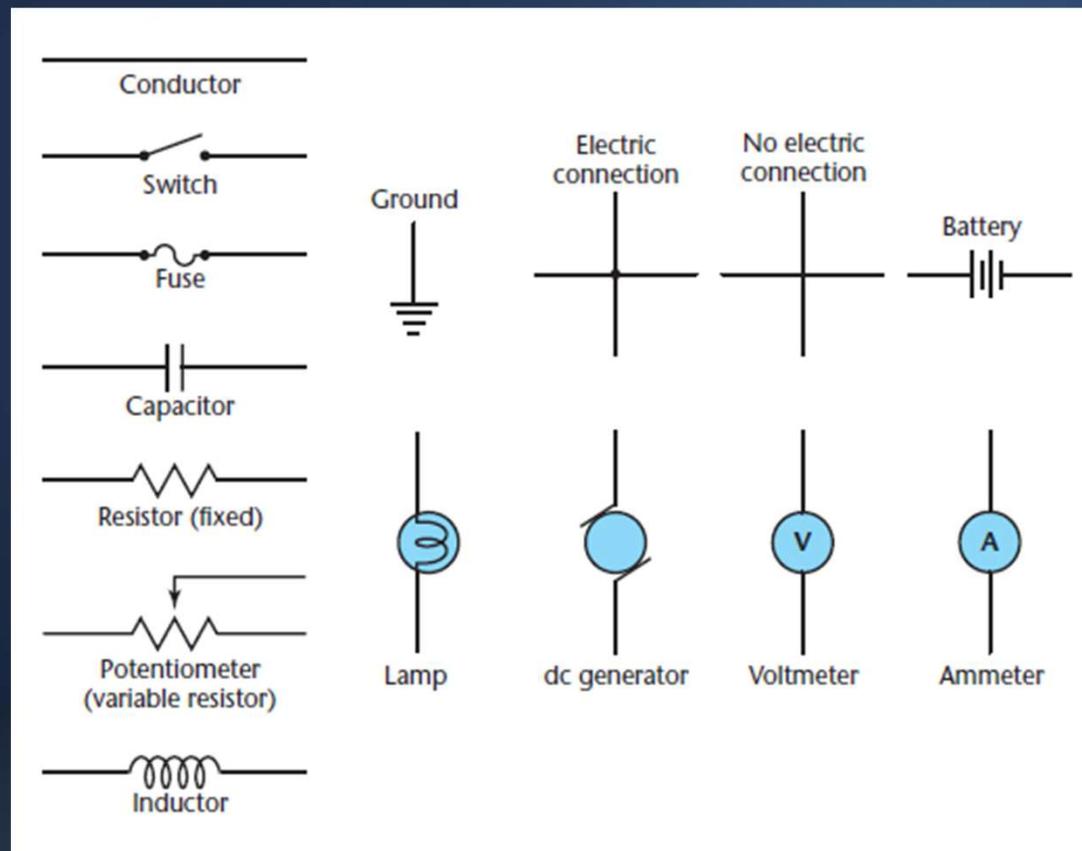

Types of Circuits

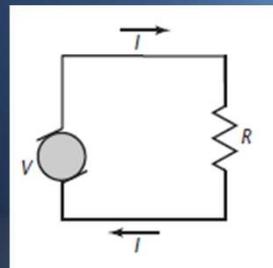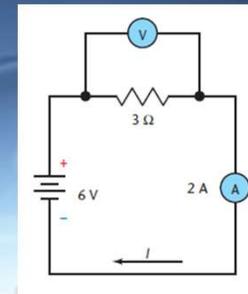- Parallel Circuits
 - Multiple paths for current to flow
- Series Circuits
 - One current path



Series Circuit

- Imagine a Series Circuit as a Mountain River with random rapids
 - Water flow is current
 - Water falls are resistors
 - Height difference between Water falls is potential difference



Series Continued


- Water flow is the current
 - The amount of water never changes as it flows down the mountain
- Charge is conserved so what charge enters must also leave
 - Therefore: current is consistent throughout the circuit



Series Continued

- The total height of the mountain is the same as the sum of the heights between the water falls
- Voltage at the source is equal to the sum of the voltage drops at each resistor
 - $V_{(\text{source})} = V_A + V_B \dots$
- Current is found by dividing the Voltage at the source by the sum of the resistors
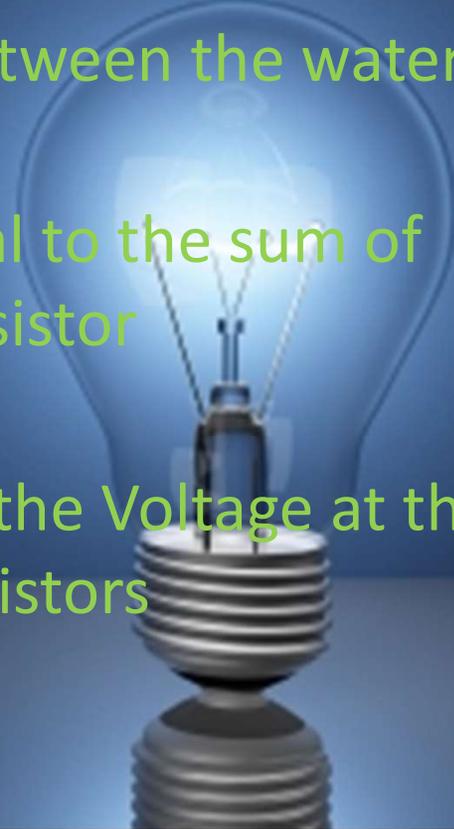
$$I = V_{(\text{source})} / (R_A + R_B)$$





Series Continued


- Equivalent resistance is the sum of all the individual resistances
- In a series, all resistors are weighted equally
 - $R_{\text{total}} = R_A + R_B + \dots$
- If more resistors are added without a change in voltage, the current decreases




Ohm's Law Triangle

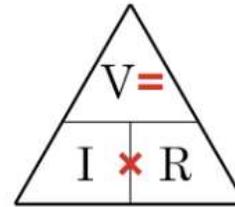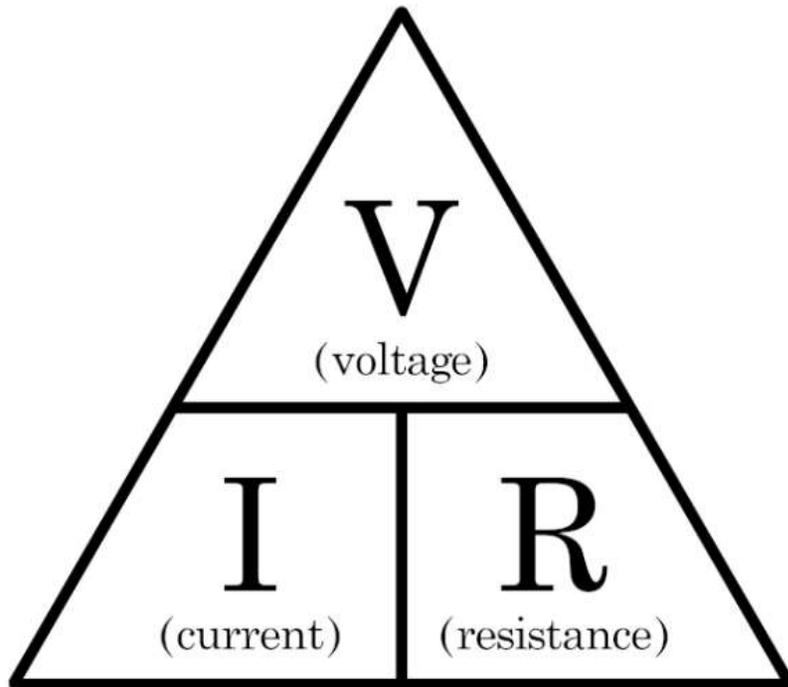

$$V = I \times R$$

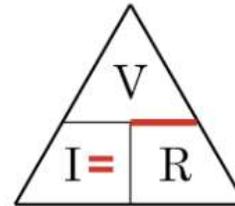

$$I = V \div R$$

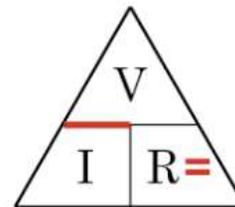


$$R = V \div I$$



Series Voltage Divider

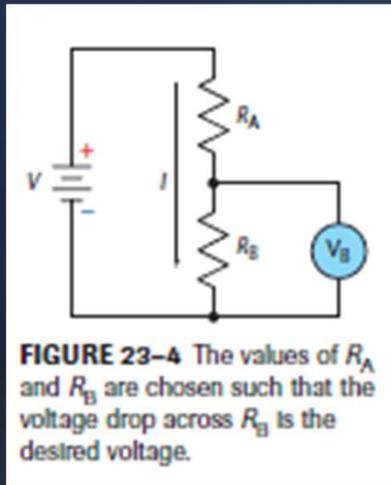- Used to produce a smaller voltage from a higher-voltage battery
 - Ex: You need 5 V of energy but have a 9V battery



Thursday / Friday (Feb 19 & 20)

- Major Grade (CER) Lab

- T:**6D** - Analyze, design, and construct series and parallel circuits using schematics and materials such as switches, wires, resistors, lightbulbs, batteries, voltmeters, and ammeters.

6E - Calculate current through potential difference across, resistance of, and power used by electrical circuit elements connected in both series and parallel circuits using Ohm's law.

- O: I will practice with real series circuits
- D: by conducting a lab and writing a CER for a major grade.
- A: series circuits, current, voltage, resistance.
- Y: What is the relationship between resistance and current in a series circuit?